

EIE2100 cheat sheet

C1. free electrons? { conductor ✓
insulator x

$$\text{Resistance (R)} = \frac{\rho L}{A} (\Omega)$$

$$\text{Conductivity (G)} = \frac{1}{R} (\text{or } S) \text{ mho siemens}$$

resistor { Wirewound
composite (carbon film)
variable resistor: potentiometer (abbr. pot)
3 terminal, middle = sliding contact/wiper


C2. DC circuit only { const. V src.
const. C src.
resistors

C3. { branch = connected to 2 nodes of a circuit
node:
loop: any closed path in a network
(essential) mesh = a loop that cannot be divided into smaller

analysis { ① Mesh-current Method: use KVL, get currents, V_{TH} , V_{OC}
② Node-Voltage Method: use KCL, get voltages, I_{out} , I_{in}
③ Superposition theorem: separately compute: Power source


circuit simplification (focus on ext. behavior) { Thevenin theorem \rightarrow V_{TH}
Norton theorem \rightarrow I_N
If contain dependent source = V_{TH} : remove load; R_{TH} : remove power source. (⊖ = short, ⊕ = break)
 I_N : short-circuit load R_{TH} : remove power source.

Max. Power Transfer

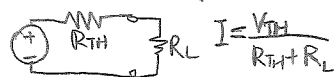

$$P_L = I^2 R_L = \frac{V_{TH}^2 R_L}{(R_S + R_L)^2} \quad (R_S = R_{TH})$$
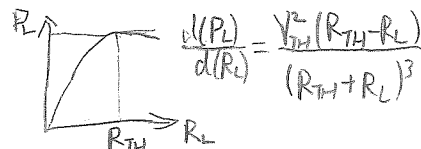
$$= \frac{V_{TH}^2 R_L}{(R_S - R_L)^2 + 4R_S R_L} = \frac{V_{TH}^2}{\left(\frac{R_S}{R_L} - \sqrt{R_L}\right)^2 + 4R_S}$$



1 2 3	1 2 3	ABC	?-M-MBY-MXC
4 5 6	4 5 6	DEF	?-M: Ans+MCD-MAY
7 8 9	7 8 9	GHI	?-M: Ans+MAX-MBD
10 11 12	10 11 12	JKL	

C4. capacitor: store energy in the electric field between " " " "

capacitance = Farad (F)
symbol: $\frac{1}{\mu}$ $\frac{1}{n}$ $\frac{1}{p}$ $\frac{1}{m}$ $\frac{1}{k}$ $\frac{1}{M}$


type { poly styrene ~ [proj] High precision (1% ~ 2%), high isolation (with its size) (30V ~ 630V)
Ceramic ~ [cons] Small c. coil structure (high L)
Electrolytic ~ [made] 2 foil separated by a thin plastic film, then roll up. 10pF ~ 1mF

app. { electronic circuit { Freq filter (with R&L, to filter certain f)
power electronic { AC to DC rectifier (shape the DC from flash lamp on camera)
large electrical sys { Power factor converter

$$Q = VC, \Rightarrow i = C \frac{di}{dt} \quad V_L = L \frac{di}{dt}$$


$$(KCL) \tau = RC \quad (KVL) \tau = L/R$$

Universal time constant method =

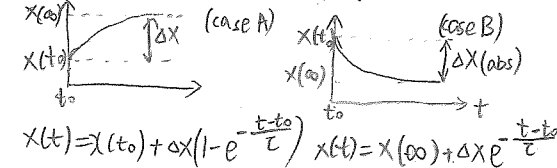


$$x(t) = x(t_0) + \Delta x (1 - e^{-\frac{t-t_0}{\tau}}) \quad x(t) = x(\infty) + \Delta x e^{-\frac{t-t_0}{\tau}}$$


C5 Amplification

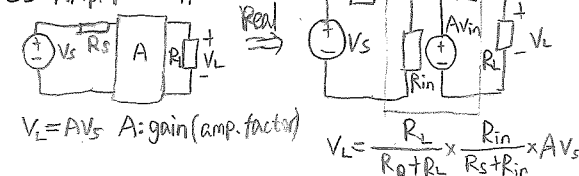


Ideal: $R_{in} \gg R_S, R_L \gg R_{out}$

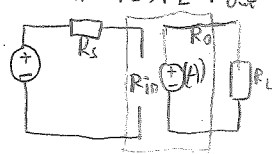

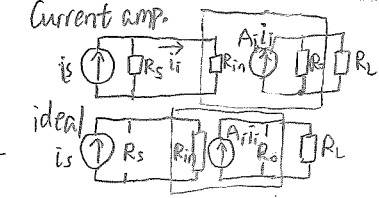Ideal Amp { $A = \infty$
 $R_{in} = \infty$
 $R_o = 0$
Bandw = ∞
 $V_o = 0$ for $V_i = V_{to}$ (input offset V)



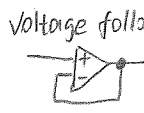Op-Amp: Near ideal, signal conditioning, filtering, math ops. (use with ext. feedback components to determine operations)




Negative feedback \Rightarrow Inverted Amp

$$i_{in} = \frac{V_{in}}{R_1}$$

$$V_o = -R_F i_{in} = -\frac{R_F}{R_1} V_{in}$$

$$A = -\frac{R_F}{R_1}$$

Non-Inverting Amplifier

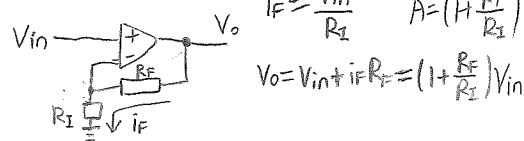


$$i_F = \frac{V_{in}}{R_1}$$

$$A = (1 + \frac{R_F}{R_1})$$

$$V_o = V_{in} + i_F R_F = (1 + \frac{R_F}{R_1}) V_{in}$$

Inverting Amp. with T-Network

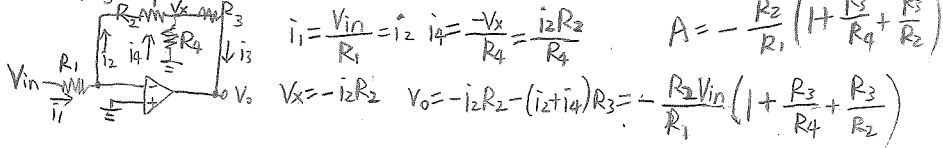


$$i_1 = \frac{V_{in}}{R_1} = i_2 = i_4 = \frac{-V_x}{R_4} = \frac{i_2 R_2}{R_4}$$

$$A = -\frac{R_2}{R_1} (1 + \frac{R_3}{R_4} + \frac{R_3}{R_2})$$


$$V_x = -i_2 R_2 \quad V_o = -i_2 R_2 - (i_2 + i_4) R_3 = -\frac{R_2 V_{in}}{R_1} (1 + \frac{R_3}{R_4} + \frac{R_3}{R_2})$$

Inverting Summer

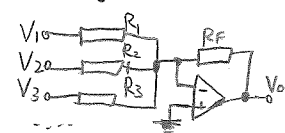

$$V_o = -\frac{R_F}{R_1} V_1 - \frac{R_F}{R_2} V_2 - \frac{R_F}{R_3} V_3 \dots$$


Differentiator

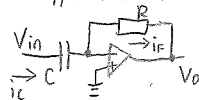

$$i_c = C \frac{dV_{in}}{dt} = i_F$$

$$V_o = -i_F R = -R C \frac{dV_{in}}{dt}$$


Integrator

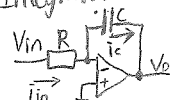

$$i_{in} = \frac{V_{in}}{R} = i_c = C \frac{d(-V_o)}{dt}$$

$$V_o = -\frac{1}{CR} \int V_{in} dt$$

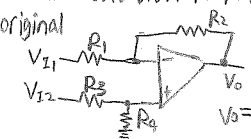
Instrumentation Amplifier $R_2 = R_3 + R_4$



$$R_1 = \frac{V_{I1}}{I_1} = \frac{V_{I1} R_1}{V_{I1} - V_{I2}} = \frac{V_{I1} R_1}{V_{I1} - V_{I2} \cdot \frac{R_2}{R_3 + R_4}}$$

$$V_o = -\frac{R_2}{R_1} V_{I1} + \frac{V_{I2} R_2}{R_3 + R_4} (\frac{R_1 + R_2}{R_1}), V_o = \frac{R_2}{R_1} (V_{I2} - V_{I1}) \text{ (if } \frac{R_1}{R_2} = \frac{R_3}{R_4})$$

(after insert V follower)

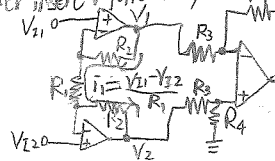


$$V_1 = V_{I1} + \frac{R_2}{R_1} (V_{I1} - V_{I2}) \quad V_2 = V_{I2} - \frac{R_2}{R_1} (V_{I1} - V_{I2})$$

$$V_o = -\frac{R_4}{R_3} (V_2 - V_1) = \frac{R_4}{R_3} (1 + \frac{R_2}{R_1}) (V_{I2} - V_{I1})$$

R_4 won't have to be that large to have large gain; low offset voltage; $R_1 = R_2 = \infty$ (low noise); high CMRR (common mode rejection ratio)



Comparator

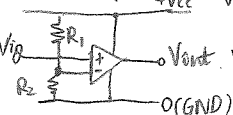

$$V_{in} > \frac{R_2 V_{cc}}{R_1 + R_2} \Rightarrow V_{out} = V_{cc}$$

$$V_{in} < \frac{R_2 V_{cc}}{R_1 + R_2} \Rightarrow V_{out} = 0 = V_{ee}$$

Rectangular Wave Generator

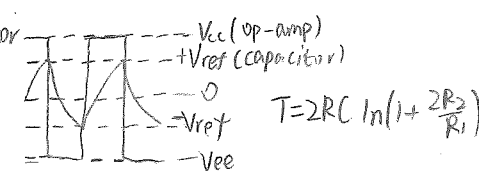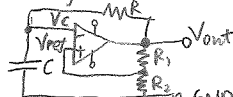

(6) AC: V alternating in polarity { electric generator, motor, power distribution system for more efficient than DC (power loss $I^2 R$, $P = VI \Rightarrow I \propto \sqrt{P}$) } predominantly used in high power app.



Newly: HVDC (solid-state power electronic, DC-AC/AC-DC converter with high ϵ)
 $DC \rightarrow AC \rightarrow HVDC$ (long) pros. lower cable P loss; smaller power tower; less loss
 $AC \rightarrow DC$ cons. very expensive ($> \$800/km$)

(6b) Phasor $Ae^{j\omega t} = A \cos(\omega t) + j \sin(\omega t) \Rightarrow Ae^{j(\omega t + \theta)} = A(\cos(\omega t + \theta) + j \sin(\omega t + \theta))$ Phasor: $Ae^{j\theta}$

let $x = A \cos(\omega t + \theta)$, $\bar{x} = Ae^{j\theta}$

$$x' = \text{Re}(Ae^{j(\omega t + \theta)})' = A \omega \cos(\omega t + \theta + \frac{\pi}{2})$$

$$\bar{x}' = A \omega e^{j(\theta + \frac{\pi}{2})} = j A \omega e^{j\theta} = j \omega \bar{x}$$

for inductor: $\bar{v}_L = L \frac{di}{dt} = \omega L I e^{j(\omega t + \frac{\pi}{2})}$

$$\bar{v}_L = j \omega L \bar{i} = j \omega \bar{v}$$

(delay I , lead V)

for capacitor: $\bar{i}_C = C \frac{dv}{dt} = \omega C V e^{j(\omega t + \frac{\pi}{2})}$

$$\bar{i}_C = \frac{1}{j \omega C} \bar{v} = -\frac{j}{\omega C} \bar{v} = \frac{\bar{v}}{j \omega C}$$

(delay V)

Impedance: $\bar{Z} = \frac{\bar{V}}{\bar{I}} = R + jX$ Resistance Reactance

Admittance: $\bar{Y} = \frac{1}{\bar{Z}} = \frac{1}{R + jX}$

Inductor: $\bar{Z} = \frac{\bar{V}}{\bar{I}} = j \omega L$

Resistor: $\bar{Z} = \frac{\bar{V}}{\bar{I}} = R$

Capacitor: $\bar{Z} = \frac{\bar{V}}{\bar{I}} = \frac{1}{j \omega C} = -\frac{j}{\omega C}$

Power: $\bar{v}(t) = I_{max} \sin(\omega t)$
 $\bar{i}(t) = I_{max} \sin(\omega t + \theta)$
 $P(t) = \frac{1}{2} I_{max}^2 \sin(2\omega t + \theta)$
 $\bar{v}(t) = -I_{max} \sin(\omega t)$
 $P(t) = -\frac{1}{2} I_{max}^2 \sin(2\omega t)$

reactive [VAR] $= I_{rms}^2 X$ App. React
true $\sim [W] = I_{rms}^2 R$
apparent [VA] $= I_{rms}^2 |Z|$
power factor $= \cos \theta$

to correct: C should be parallel voltage drops need to break the circuit; with inductive load for: short circuit lead to blow of them

(7) transformer: 2 magnetically coupled inductors, for AC voltage step up/down, circuit isolation, impedance matching

Impedance transformation eg. audio transformer for impedance matching & galvanic isolation