

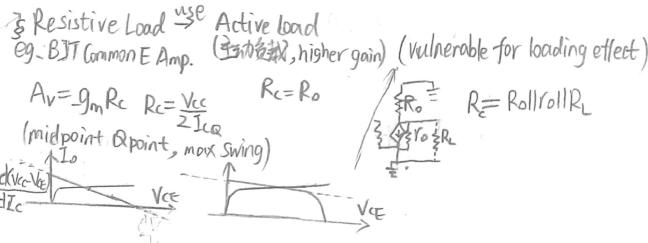


§ IC Design Philosophy = minimize size, power

- (large & med Resistors & Capacitors use Transistors)
- biasing Resistors use const current source
- Coupling/Bypass Capacitors use direct coupling techng
- power supply $\approx 1V$ (aviod breakdown thin oxide layer)
- \Rightarrow transistor overdrive voltage $0.1V \sim 0.2V$ only
- Device Variety
- BJT: special analog applications (eg. HQ OpAmp)
- Complementary MOS: compatibility with digital, photosensitive

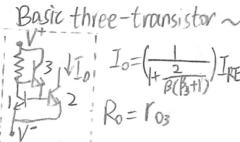

§ IC Biasing Using const. Current Source

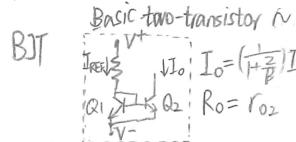

Cascade Current Source

$$I_{E3} = I_{REF}(\beta_2 + 1) \quad (A)$$

$$I_{C1} = I_{C2} = I_{E4} = \frac{I_{E3}}{\beta_3 + 2} \quad (B)$$

$$I_{REF} = I_{C1} + I_{C2} = \frac{I_{E3}}{\beta_3 + 1} + \frac{I_{E3}}{\beta_3 + 2} \quad (C)$$

$$I_{E4} = \frac{I_{E3}\beta_3}{\beta_3 + 1} = \frac{\beta_1\beta_3}{\beta_3 + 2} I_{REF} \approx g_m r_{in} r_{out} = \beta I_{ref}$$

Basic two-transistor MOSFET

 $I_{REF} = k_{n1}(V_{DS1} - V_{TN})$

MOSFET Current mirror (with MOSFET Ref. current)

 $V_{DS3} + V_{DS1} = V^+ - V^-$
 $I_{REF} = k_{n1}(\frac{W}{L})(V_{DS1} - V_{TN})$
 $I_{DS3} = k_{n3}(\frac{W}{L})(V_{DS3} - V_{TN})^2$
 $X(V_{DS1}V_{TN}) = V^+V^- - V_{DS1}V_{TN} \Rightarrow V_{DS3} = \frac{V^+ - V^- + (x-1)V_{TN}}{Hx}$

Cascode MOSFET \sim

 $I_{ref} = R_o = r_{o2} + r_{o4}(1 + g_m r_{o2}) \approx g_m r_{o2} r_{o4}$

Wilson Current Source

$$I_o = \frac{P_3}{P_3 + 1} I_{E3} \quad I_{C2} = I_{C1} = \frac{\beta_1 I_{E3}}{\beta_2 + 2} \quad R_o = \frac{\beta_1 R_o}{2}$$

$$I_{REF} = I_{C1} + I_{C2} = \frac{\beta_1(\beta_3 + 1)}{(\beta_2 + 2)\beta_3} I_o$$

Widlar Current Source

 $I_{REF} = I_o = \frac{V_{CE1} - V_{CE2}}{V^+ - V^-} \quad R_o = (R_{e1}||r_{T2}) + r_{o2} + (R_{e2}||r_{T1})g_m r_{o2}$

Mutitransistor \sim

 $I_o = I_{o2} = \frac{I_{REF}}{H(HN)}$

Multiputput \sim

 $I_o = I_{o1} = \frac{N_i I_{REF}}{H(HN)}$

§ Differential Amplifier (Diff-Amp 差分放大器)

$V_o = A_{vD}(V_1 - V_2)$ $V_i = V_{cm} + \frac{V_d}{2}$ $V_d(A_D)$ Direct Analysis

Basic BJT Differential Pair

$$\begin{aligned} V^+ &\xrightarrow{\text{BJT}} V_o = A_{vD}(V_1 - V_2) \\ V_i &= V_1 - V_2 = 2V_{cm} + V_d + V_2 = V_{cm} + \frac{V_d}{2} \\ V_d(A_D) &\text{ Direct Analysis} \\ I_1 &= I_{SC} \frac{V_{BE1}}{V_i} \quad I_2 = I_{SC} \frac{V_{BE2}}{V_i} \\ I_1 &= I_{SC} \frac{V_{BE1}}{V_{BE1} + V_{BE2}} = I_{SC} \frac{V_{BE1}}{V_{BE1} - V_{BE2}} = I_{SC} \frac{V_{BE1}}{V_{BE1} - V_{BE2} - V_d} \\ I_2 &= I_{SC} \frac{V_{BE2}}{V_{BE1} - V_{BE2} - V_d} \end{aligned}$$

Small-signal (Ad)
 AC Equi.
 Half circuit
 Analysis

$R_{in,d} = \frac{V_{BE1}}{I_{SC}}$ to increase $R_{in,d}$

$R_{id} = 2R_{in,d}$ $R_{id} = 2(R_{in} + (H\beta)R_E)$

