

L1

history  
 1904 Fleming = diode vacuum tube  
 1925 Lilienfeld = field-effect device  
 1947 3 people at Bell Lab = BJT  
 1958 IC 1961 commercial digital IC  
 1968 op-amp (UA709) → Fairchild Semi.  
 1970 IBM = 1-transistor dy. memory cell  
 1971 Intel = 4004 microprocessor  
 1981 1Mb memory  
 2009 Kao = Charge-Coupled Device (CCD) in optical communication

Foreign Spectrum of signals  
 (characterize periodic signals)  
 Representing a  $v_s(t)$  or  $i_s(t)$  as  
 $\sum A_n \sin(\omega_n t + \phi_n)$   
 ex. wave  $V(t) = \frac{4V}{\pi} (\sin \omega t + \frac{1}{3} \sin 3\omega t + \dots)$

L2

Signal Processing Problem: some signals too small for reliable processing ⇒ Signal Amp  
 Problem: Non-linear =  $v_o(t) = A_1 v_i(t) + A_2 v_i^2(t)$ , lead to distortion unwanted

Signal Amp  
 linear:  $A = \frac{y}{x}$  (large or small weak)  
 non-n:  $A = \frac{dy}{dx}$  (only small) Q-point

Voltage gain  $A_v = \frac{V_o}{V_i}$  in dB =  $20 \log_{10} |\frac{V_o}{V_i}|$   
 Current gain  $A_i = \frac{I_o}{I_i}$  =  $20 \log_{10} |\frac{I_o}{I_i}|$   
 Power gain  $A_p = \frac{V_o I_o}{V_i I_i} = A_v A_i$  =  $10 \log_{10} |A_p|$

Energy =  $P_{dc} + P_I = P_L + P_{dis}$   
 $P_{dc} = V_{CC} I_{CC} + V_{EE} I_{EE}$   
 DC deliver energy for amplification  
 $P_I$ : from signal  $\eta = \frac{P_L}{P_{dc}}$   
 $P_L$ : to load  
 $P_{dis}$ : consumed by amplifier

Amplifier saturation  
 Output voltage should remain in a region (eg. powered by DC supply)  
 $\Rightarrow \frac{L}{A_v} \leq V_i \leq \frac{L}{A_v}$

Amplifier Symbol convention  
 $I_c$ : DC component  
 $i_c$ : AC component  
 $i_c$ : total instan. value  
 $I_c$ : peak amplitude/phase

Amp type  
 ① Voltage ~  $\frac{V_o}{V_i}$   
 ② Current ~  $\frac{I_o}{I_i}$   
 ③ Transconductance ~  $\frac{I_o}{V_i}$   
 ④ Transresistance ~  $\frac{V_o}{I_i}$

L3

Diode  
 P-N Junction  
 anode cathode  
 $I_D = I_S [e^{\frac{V_D}{V_T}} - 1]$   
 $V_T = \frac{kT}{q}$  (Thermal voltage)  
 $k$ : Boltzman const  $q$ : charge  
 $V_T(300K) = 0.026V$   
 $n$  (Ideality factor,  $1 \leq n \leq 2$ )  
 $I_S$  (Sat. Current) Silicon  $10^{-15} \sim 10^{-13} A$  (Rev. I drift)

Reverse-bias  $i_D = -I_S$   
 Forward-bias  $i_D = I_S [e^{\frac{V_D}{V_T}} - 1]$   
 dead zone

Ideal Diode Model  
 Idealize  $V_D < 0 \Rightarrow i_D = 0$   
 $V_D = 0 \Rightarrow i_D \geq 0$   
 $V_D > 0 \Rightarrow i_D \geq 0$

Piecewise-Linear Model  
 Reverse-bias  $V_D < V_T \Rightarrow i_D = 0$   
 Forward-bias  $V_D \geq V_T \Rightarrow i_D = I_S e^{\frac{V_D - V_T}{V_T}}$   
 slope =  $\frac{1}{V_T}$   
 (0.2~0.3V Ge)  
 (0.6~0.7V Si)

Analysis:  
 ① DC:  $V_D = V_T$  or  $0 \leq V_D < V_T$  OFF  
 (Assumption, trial-and-error)  
 ② AC:  $\rightarrow \rightarrow \rightarrow$  (OFF) or  $\rightarrow \rightarrow \rightarrow$  (ON)

L4

Semiconductors  
 Single-element  
 Compound  
 P-N Junction

$T = 300K$  thermal generation → covalent bond broke  
 → free electrons & holes → til  $V_{generation} = V_{recombine}$   
 →  $p(n)$  const (p may  $\neq n$ , however too small for intrinsic)  
 Sol: Dope impure atoms (B for N-type, P for P-type, small amount) (more hole) (more electron)

Electron (doped diffusion,  $I_D$ )  
 External (minor) thermal-drift ( $I_S$ )  
 Space charge region (depletion region)  
 $U_{ho}(-U)$   
 $U_{ho}(-U)$   
 $I_D$   
 $I_S$   
 $q$ : charge  
 $p(n)$ : density  
 $\mu$ : mobility

VR (Reverse bias)  
 ① Avalanche Breakdown  $\rightarrow V_{BR} \rightarrow E_k = qV_d$   
 Low doping density, enough -U and PNJ length  $\rightarrow \approx$  Tevatron  
 → high speed e. easier to activate valence e. & c. bond  
 → original e. & activated e. h. pair → activate more e. h. pair  
 ② Zener Breakdown  $\rightarrow$  Same  $V_{int}$  lower  $L_{PNJ}$ , higher  $E_{int}$   
 High doping density → valence e. activated (no need too high  $U_{ext}$ )  
 ③ Thermal Breakdown (irreversible, 热击穿, 二次击穿)

L5

Diode  
 ① AC → DC Rectifier  
 Application:  $V_i \rightarrow V_s \rightarrow V_o$   
 Lowpass, reduce ripple  
 Keep  $V_{out}$  for different  $R_L$

Half-wave  $V_o$   
 Full-wave  $V_o$   
 Filter (Remove Ripple)  
 $V_r \approx V_p - V_p e^{-\frac{1}{RC}}$   
 $\approx V_p (1 - \frac{1}{RC} e^{-\frac{1}{RC}})$   
 $\approx V_p \frac{1}{RC} = \frac{V_p}{RC}$  (Full-w)  
 $\approx \frac{V_p}{RC}$  (H.w)

② Zener Diode Circuit  
 ③ Clipper circuit  
 ④ Clamper Circuit (shift)  
 ⑤ Detector Circuit  
 ⑥ Logic Gate  
 $V_1 \rightarrow V_o$  (OR)  
 $V_2 \rightarrow V_o$  (AND)  
 $V_1, V_2 \rightarrow V_o$  (AND)  
 $V_1, V_2 \rightarrow V_o$  (AND)

L6 Transistors { Bipolar Junction Transistor (BJT) 双极型晶体管 } { Junction MOSFET 结型场效应管 } { Insulated Gate MOSFET (IGMOSFET) 绝缘栅型场效应管 }  
 (3-terminal) { Metal Oxide Semiconductor Field Effect Transistor (MOSFET) 金属氧化物半导体场效应晶体管 (MOS管) } { n-channel (Enhancement Mode) ~ n沟道(增强型) } { p-channel (~) ~ p沟道(~) }

BJT { npn type } { pnp type }

When active:  $\odot$  in E diffuse to C (high n  $\rightarrow$  low n).  
 $\rightarrow$  til recombine of  $\odot$  in P form barrier  
 $\rightarrow$  for each  $\odot$  pick up by base  $\rightarrow$  barrier temp. fall  
 $\rightarrow$  E  $\odot$  C diffuse temp. cont.  $\rightarrow$   $\beta$   $\odot$  s can diffuse to C

Mode of Operation: Cutoff, Active, Sat.

BE BC npn status:  $V_B - V_{BE(on)} < V_E$ ,  $V_C > V_B - V_{BE(on)}$ ,  $V_B - V_{BE(on)} > V_E$   
 pnp status:  $V_B + V_{BE(on)} > V_E$ ,  $V_C < V_B + V_{BE(on)}$ ,  $V_B + V_{BE(on)} < V_E$

$I_C = I_S e^{\frac{V_{BE}}{V_T}} (1 + \frac{V_{CE}}{V_A})$  Early effect  $\rightarrow r_o$   
 $\frac{1}{r_o} = \frac{\partial I_C}{\partial V_{CE}} \bigg|_Q = \frac{I_S e^{\frac{V_{BE}}{V_T}}}{V_A} = \frac{I_{CQ}}{V_A}$  in AC:  $\frac{1}{r_o} \approx \frac{1}{V_A}$

C-V/load line of C-E on BJT

Voltage Transfer Curve

Bias stability ( $V_{CEQ}$ ) (upon  $\beta$  change)  
 For fixed  $V_{CC}, V_{EE}, V_{BB}, R_B, R_C, R_E$ , variable  $\beta$ . If  $I_{CQ} \approx I_{EQ} \rightarrow$  stable:  
 $\Rightarrow V_{CEQ} \rightarrow$  stable  
 So, from  $I_{CQ} = \beta I_{BQ} = \frac{\beta(V_{BB} - V_{EE} - V_{BE(on)})}{R_B + (\beta + 1)R_E}$   
 Introduce neg. feedback  $V_{EE}$  let  $R_E \gg \frac{R_B + (\beta + 1)R_E}{\beta}$   
 $I_{CQ} \rightarrow V_{CEQ} \rightarrow V_{RB} \rightarrow I_{BQ} \rightarrow V_{CEQ}$

L7 BJT Analysis: ① DC ( $I_{BQ}, I_{CQ}, V_{CEQ}$ )  
 ② AC ( $r_{\pi}, g_m, R_i, r_o, R_o, A_v, A_i$ )

BJT Amp. Conf.

- ① Common Emitter:  $A_v > 1, A_i > 1$ , mod  $R_i$ , mod to high  $R_o$
- ② Common Collector (Emitter Follower):  $A_v \approx 1, A_i > 1$ , high  $R_i$ , low  $R_o$
- ③ Common Base:  $A_v > 1, A_i \approx 1$ , low  $R_i$ , mod to high  $R_o$

L8 IGMOSFET

When  $U_G < U_{TN}$ ,  $\downarrow \uparrow \odot$  in P  $\rightarrow$  PNJ forms below G (in B)  
 when  $U_G > U_{TN}$ , n-channel between S, D forms below G above PNJ (in B)

$I_D$  forms when  $U_{GS} > 0$   
 non-sat.  $I_D = K_n [2(U_{GS} - U_{TN})U_{DS} - U_{DS}^2]$   
 $[K_n] = A/V^2$   
 Sat.  $I_D = K_n (U_{GS} - U_{TN})^2$   
 Early Effect:  $\frac{1}{r_o} = \frac{\partial I_D}{\partial U_{DS}} \bigg|_Q = \lambda I_{DQ} = \frac{I_{DQ}}{V_A}$

Bias-Stable:  $V_D = V^+ - R_D I_{DQ}$ ,  $V_S = R_S I_{DQ} + V^-$   
 $I_{DQ} = K_n (V_G - U_{TN} - R_S I_{DQ})^2$

L9 IGMOSFET Analysis ① DC ( $V_{GSQ}, V_{DSQ}, I_{DQ}$ )  
 ② AC ( $g_m, R_i, r_o, R_o, A_v, A_i$  (Common))

IGMOSFET Amp. Conf.

- ① Common-Source:  $A_v > 1, R_i = R_{TH}$ , Mod to high  $R_o$
- ② Common-Drain (Source-Follower):  $A_v \approx 1, R_i = R_{TH}$ , Low  $R_o$
- ③ Common-Gate:  $A_v > 1, A_i \approx 1$ , low  $R_i$ , mod to high  $R_o$

L10 Freq. Response

BJT

Coupling C:  $C_C$  (large),  $C_C$  (substantive)  $V_o = -\beta R_{C1} V_i = -\frac{\beta R_{C1} V_i}{(R_B + R_{iB})(R_S + \frac{1}{sC_C} + R_i)}$   
 $= -\frac{\beta R_{C1} V_i}{(R_B + R_{iB})(1 + sC_C T_s)(R_S + R_i)}$   
 $T_s = (R_S + R_i)C_C$   
 $f_L = \frac{1}{2\pi T_s}$  time const. method

FET

Am lowers 3-dB upon  $\omega = \frac{1}{T_s}$   
 $(\frac{1}{1 + sT_s}) = \frac{1}{\sqrt{2}}$   
 $f_L = \frac{1}{2\pi T_s}$